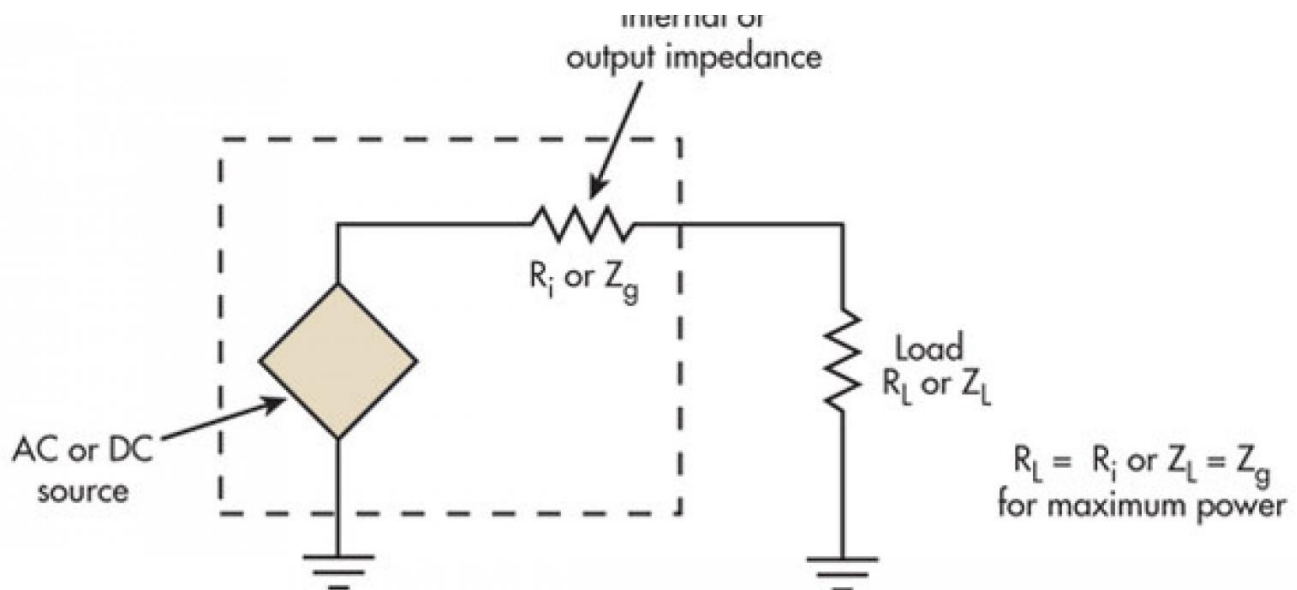


## ELECTRONIC DESIGN



TECHNOLOGIES &gt; COMMUNICATIONS

## Back to Basics: Impedance Matching (Part 1)

Lou Frenzel | Oct 24, 2011

[Download this article in .PDF format](#)

The term “impedance matching” is rather straightforward. It’s simply defined as the process of making one impedance look like another. Frequently, it becomes necessary to match a load impedance to the source or internal impedance of a driving source.

A wide variety of components and circuits can be used for impedance matching.

The maximum power transfer theorem states that to transfer the maximum amount of power from a source to a load, the load impedance should match the source impedance. In the basic circuit, a source may be dc or ac, and its internal resistance ( $R_i$ ) or generator output impedance ( $Z_g$ ) drives a load resistance ( $R_L$ ) or impedance ( $Z_L$ ) (Fig. 1):

$$R_L = R_i \text{ or } Z_L = Z_g$$



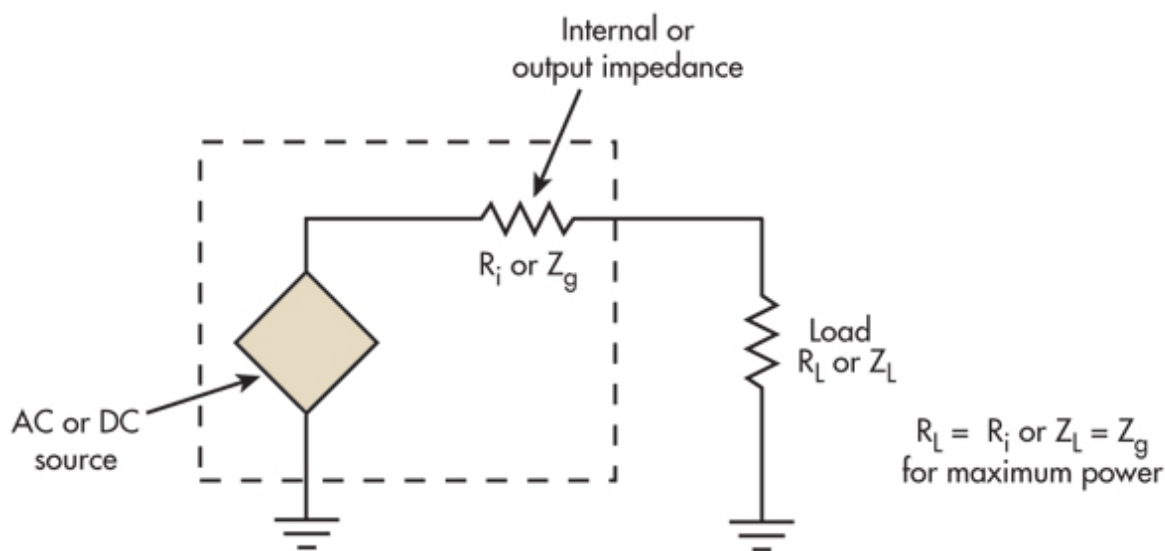


Fig 1. Maximum power is transferred from a source to a load when the load resistance equals the internal resistance of the source.

A plot of load power versus load resistance reveals that matching load and source impedances will achieve maximum power (Fig. 2).

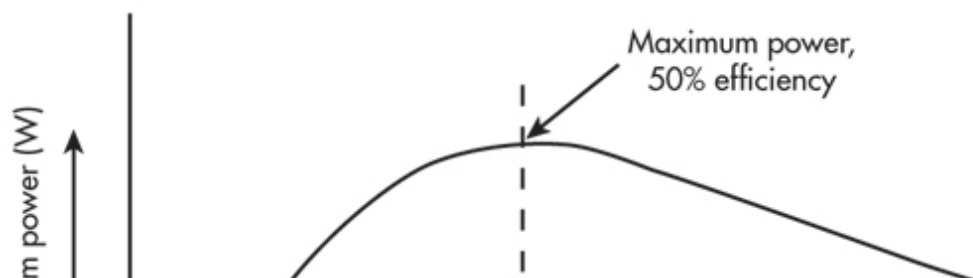

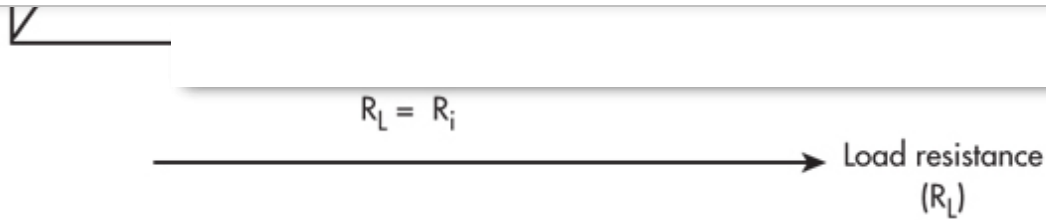

*Fig 2. Varying the load resistance on a source shows that maximum power to the load is achieved by matching load and source impedances. At this time, efficiency is 50%.*

A key factor of this theorem is that when the load matches the source, the amount of power delivered to the load is the same as the power dissipated in the source. Therefore, transfer of maximum power is only 50% efficient.

The source must be able to dissipate this power. To deliver maximum power to the load, the generator has to develop twice the desired output power.

## Applications

Delivery of maximum power from a source to a load occurs frequently in electronic design. One example is when the speaker in an audio system receives a signal from a power amplifier (Fig. 3). Maximum power is delivered when the speaker impedance matches the output impedance of the power amplifier. While this is theoretically correct, it turns out that the best arrangement is for the power amplifier impedance to be less than the speaker impedance. The reason for this is the complex nature of the speaker as a load and its mechanical response.



$$Z_L = 8 \Omega$$

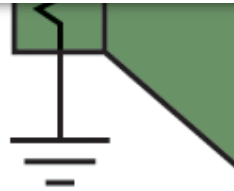


Fig 3. Unmatched impedances provide the best amplifier and speaker performance.

Another example involves power transfer from one stage to another in a transmitter (Fig. 4). The complex ( $R \pm jX$ ) input impedance of amplifier B should be matched to the complex output impedance of amplifier A. It's crucial that the reactive components cancel each other. One other example is the delivery of maximum power to an antenna (Fig. 5). Here, the antenna impedance matches the transmitter output impedance.


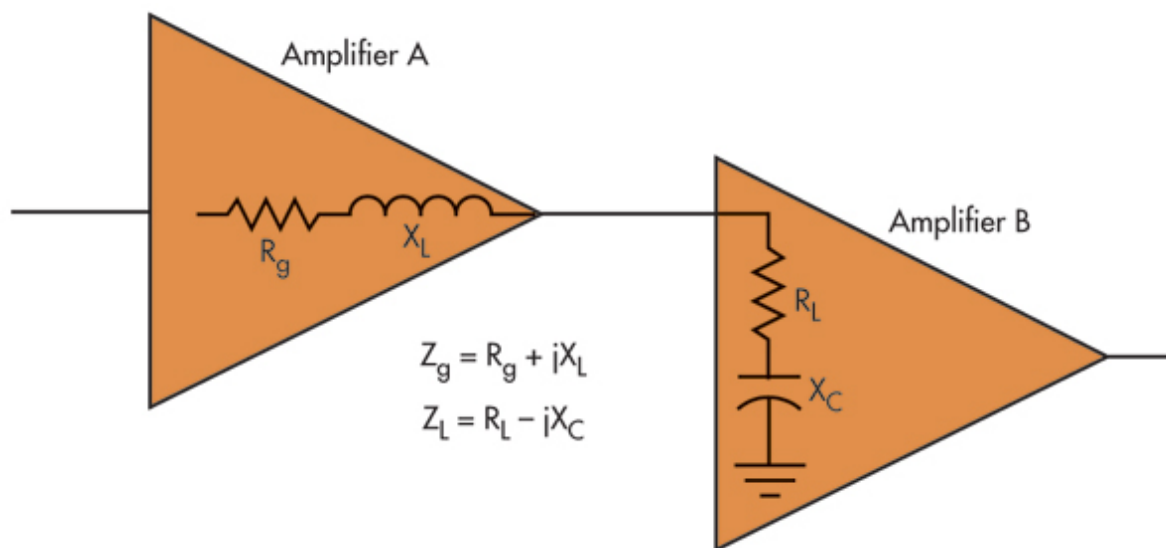


Fig 4. Impedances in radio-frequency transmitters must be matched to pass maximum power from stage to stage. Most impedances include inductances and capacitances that must also be factored into the matching process.

Transmitter  
i.f.

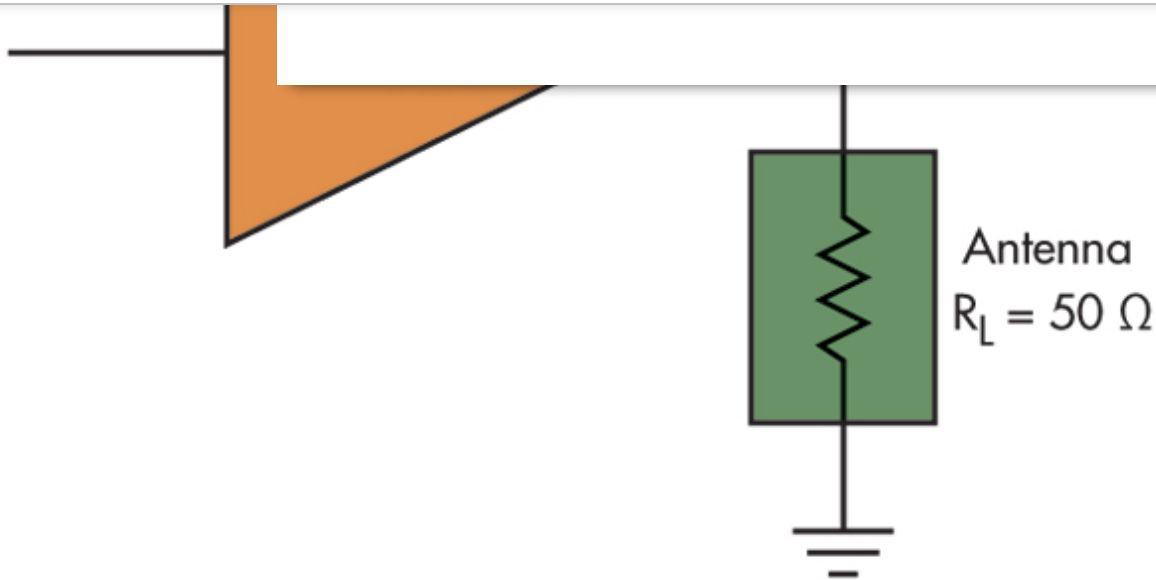

*Fig 5. Antenna impedance must equal the transmitter output impedance to receive maximum power.*

## Transmission-Line Matching

This last example emphasizes another reason why impedance matching is essential. The transmitter output is usually connected to the antenna via a transmission line, which is typically coax cable. In other applications, the transmission line may be a twisted pair or some other medium.

A cable becomes a transmission line when it has a length greater than  $\lambda/8$  at the operating frequency where:


$$\lambda = 300/f_{\text{MHz}}$$

For example, the wavelength of a 433-MHz frequency is:

$$\lambda = 300/f_{\text{MHz}} = 300/433 = 0.7 \text{ meters or } 27.5 \text{ inches}$$

A connecting cable is a transmission line if it's longer than  $0.7/8 = 0.0875$  meters

To achieve maximum power transfer over a transmission line, the line impedance must also match the source and load impedances (Fig. 6). If the impedances aren't matched, maximum power will not be delivered. In addition, standing waves will develop along the line. This means the load doesn't absorb all of the power sent down the line.

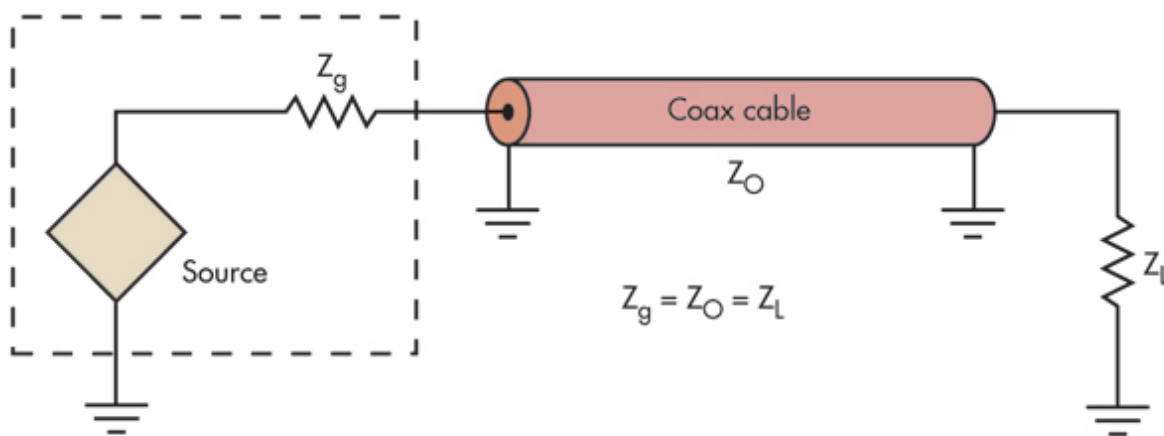

*Fig 6. Transmission lines have a characteristic impedance ( $Z_O$ ) that must match the load to ensure maximum power transfer and withstand loss to standing waves.*

Consequently, some of that power is reflected back toward the source and is effectively lost. The reflected power could even damage the source. Standing waves are the distributed patterns of voltage and current along the line. Voltage and current are constant for a matched line, but vary considerably if impedances do not match.

The amount of power lost due to reflection is a function of the reflection coefficient ( $\Gamma$ ) and the standing wave ratio (SWR). These are determined by the amount of mismatch between the source and load impedances.

$$\text{SWR} = Z_O/Z_L \text{ (for } Z_O > Z_L \text{)}$$

For a perfect match,  $\text{SWR} = 1$ . Assume  $Z_L = 75 \Omega$  and  $Z_O = 50 \Omega$ :

$$\text{SWR} = Z_L/Z_O = 75/50 = 1.5$$

The reflection coefficient is another measure of the proper match:

$$\Gamma = (Z_L - Z_O)/(Z_L + Z_O)$$

For a perfect match,  $\Gamma$  will be 0. You can also compute  $\Gamma$  from the SWR value:


$$\Gamma = (\text{SWR} - 1)/(\text{SWR} + 1)$$

Calculating the above example:

$$\Gamma = (\text{SWR} - 1)/(\text{SWR} + 1) = (1.5 - 1)/(1.5 + 1) = 0.5/2.5 = 0.2$$

Looking at amount of power reflected for given values of SWR ([Fig. 7](#)), it should be noted that an SWR of 2 or less is adequate for many applications. An SWR of 2 means that reflected power is 10%. Therefore, 90% of the power will reach the load.



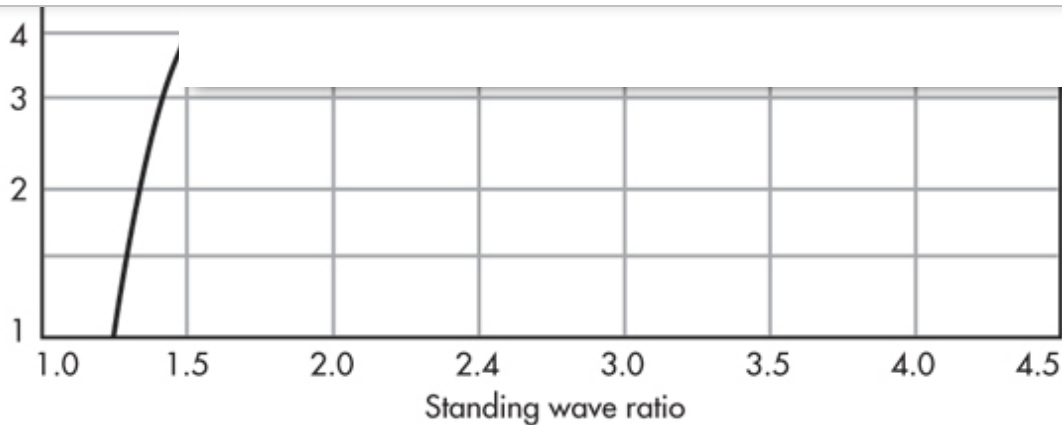

*Fig 7. This plot illustrates reflected power in an unmatched transmission line with respect to SWR.*

Keep in mind that all transmission lines like coax cable do introduce a loss of decibels per foot. That loss must be factored into any calculation of power reaching the load. Coax datasheets provide those values for various frequencies.

Another important point to remember is that if the line impedance and load are matched, line length doesn't matter. However, if the line impedance and load don't match, the generator will see a complex impedance that's a function of the line length.

Reflected power is commonly expressed as return loss ( $R_L$ ). It's calculated with the expression:


$$R_L \text{ (in dB)} = 10 \log (P_{IN}/P_{REF})$$

$P_{IN}$  represents the input power to the line and  $P_{REF}$  is the reflected power. The greater the dB value, the smaller the reflected power and the greater the amount of power delivered to the load.

## Impedance Matching




(Fig. 8). The impedance-matching circuit or component is a piece of equipment that makes the load match the generator impedance.

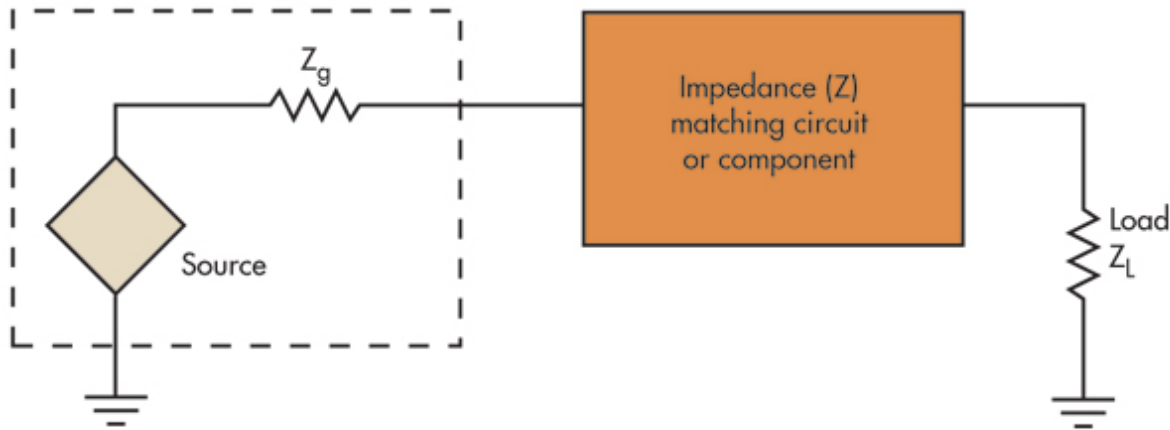

*Fig 8. An impedance-matching circuit or component makes the load match the generator impedance.*

A wide range of solutions is possible in this scenario. Two of the simplest involve the transformer and the  $\lambda/4$  matching section. A transformer makes one impedance look like another by using the turns ratio (Fig. 9):

$$N = N_s/N_p = \text{turns ratio}$$

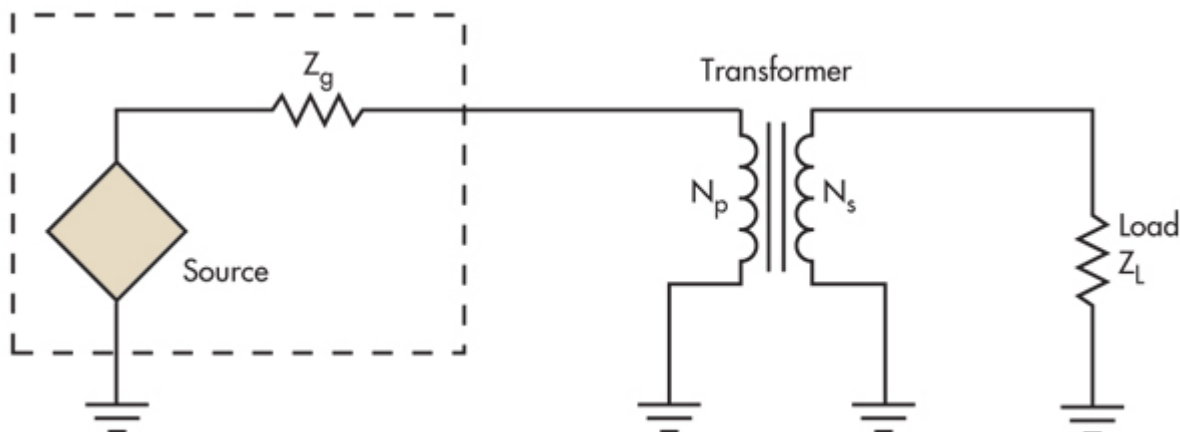

*Fig 9. A transformer offers a near ideal method for making one impedance look*

is often written a

The relationship to the impedances can be calculated as:

$$Z_s/Z_p = (N_s/N_p)^2$$

or:

$$N_s/N_p = \sqrt{(Z_s/Z_p)}$$


$Z_p$  represents the primary impedance, which is the output impedance of the driving source ( $Z_g$ ).  $Z_s$  represents the secondary, or load, impedance ( $Z_L$ ).

For example, a driving source's 300- $\Omega$  output impedance is transformed into 75  $\Omega$  by a transformer to match the 75- $\Omega$  load with a turns ratio of 2:1:

$$N_s/N_p = \sqrt{(Z_s/Z_p)} = \sqrt{(300/75)} = \sqrt{4} = 2$$

The highly efficient transformer essentially features a wide bandwidth. With modern ferrite cores, this method is useful up to about several hundred megahertz.

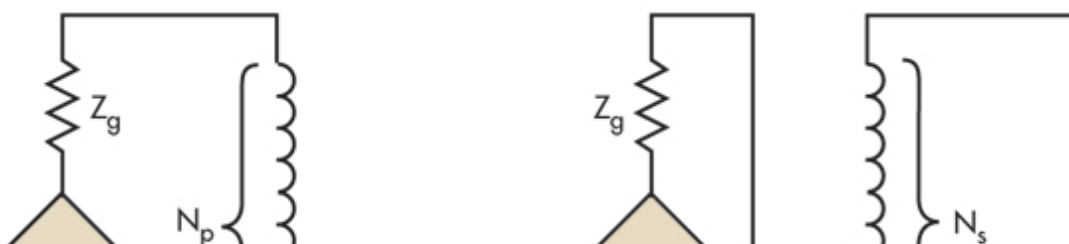An autotransformer with only a single winding and a tap can also be used for impedance matching. Depending on the connections, impedances can be either stepped down (**Fig. 10a**) or up (**Fig. 10b**).



(a)

Fig 10. A single-winding autotransformer with a tap can step down (a) or step up (b) impedances like a standard two-winding transformer.

The same formulas used for standard transformers apply. The transformer winding is in an inductor and may even be part of a resonant circuit with a capacitor.

A transmission-line impedance-matching solution uses a  $\lambda/4$  section of transmission line (called a Q-section) of a specific impedance to match a load to source (Fig. 11):

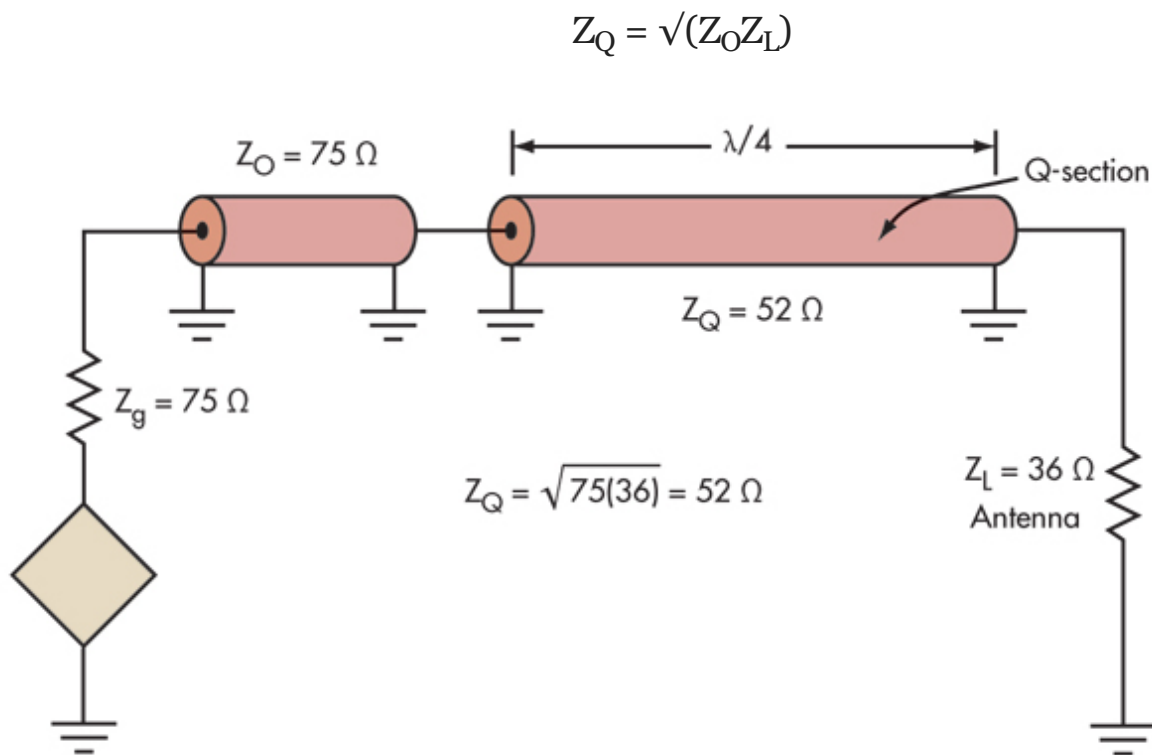


Fig 11. A  $\lambda/4$  Q-section of transmission line can match a load to a generator at one frequency.

Here, the 36- $\Omega$  impedance of a  $\lambda/4$  vertical ground-plane antenna is matched to a 75- $\Omega$  transmitter output impedance with a 52- $\Omega$  coax cable. It's calculated as:

$$Z_Q = \sqrt{(75)(36)} = \sqrt{2700} = 52 \, \Omega$$

Assuming an operating frequency of 50 MHz, one wavelength is:

$$\lambda = 300/f_{\text{MHz}} = 300/50 = 6 \text{ meters or about 20 feet}$$

$$\lambda/4 = 20/4 = 5 \text{ feet}$$

Assuming the use of 52- $\Omega$  RG-8/U coax transmission line with a velocity factor of 0.66:

$$\lambda/4 = 5 \text{ feet} (0.66) = 3.3 \text{ feet}$$

Several important limitations should be considered when using this approach. First, a cable must be available with the desired characteristic impedance. This isn't always the case, though, because most cable comes in just a few basic impedances (50, 75, 93, 125  $\Omega$ ). Second, the cable length must factor in the operating frequency to compute wavelength and velocity factor.

In particular, these limitations affect this technique when used at lower frequencies. However, the technique can be more easily applied at UHF and microwave frequencies when using microstrip or stripline on a printed-circuit board (PCB). In this case, almost any desired characteristic impedance may be employed.

The next part of this series will explore more popular impedance-matching techniques

## 6 COMMENTS

## RELATED

**Wireless Makes the Electric Grid Smarter and More Reliable (.PDF Download)**


APR 09, 2019

**SPONSORED CONTENT****Wireless Makes the Electric Grid Smarter and More Reliable**

APR 09, 2019

**Wi-Fi 6 vs. 5G: Why Trying to Pick a Winner is Missing the Point**

APR 02, 2019

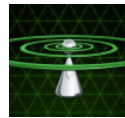**New Applications Bring Renewed Life to UWB Wireless**

APR 01, 2019

Electronic Design is a leading source of information for the electronics industry. We provide the latest news, analysis, and product information to help you stay on top of the latest trends and developments in the industry. Our content is designed to help you make informed decisions about your business and your future.

[About Us](#)[Contact](#)[Advertise](#)[Newsletter](#)[Ad Choices](#)[Privacy Policy](#)[Terms of Service](#)[Cookie Policy](#)

Follow us: